

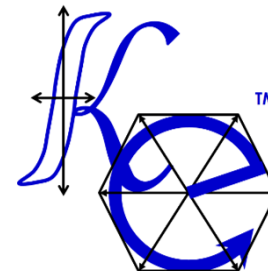
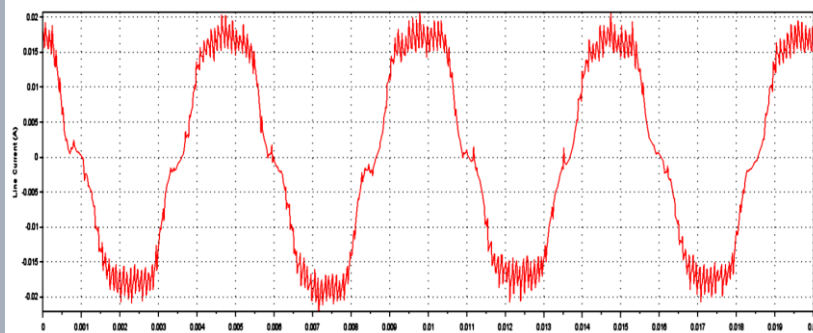
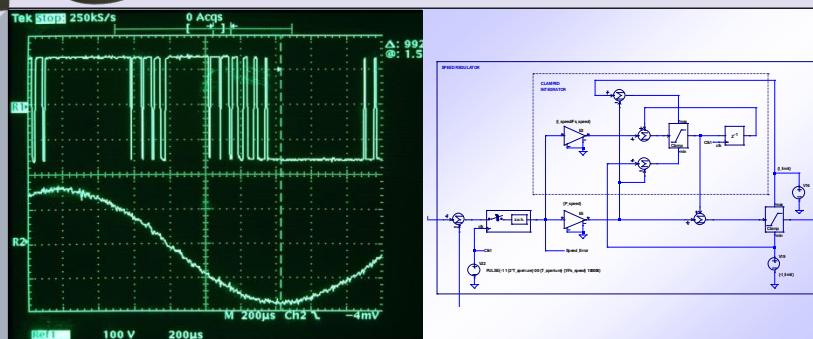


# Current Sensing

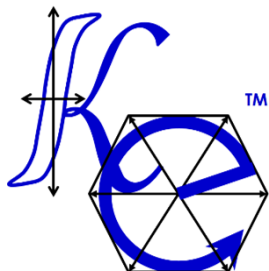

# Cycle-by-Cycle Current Limit

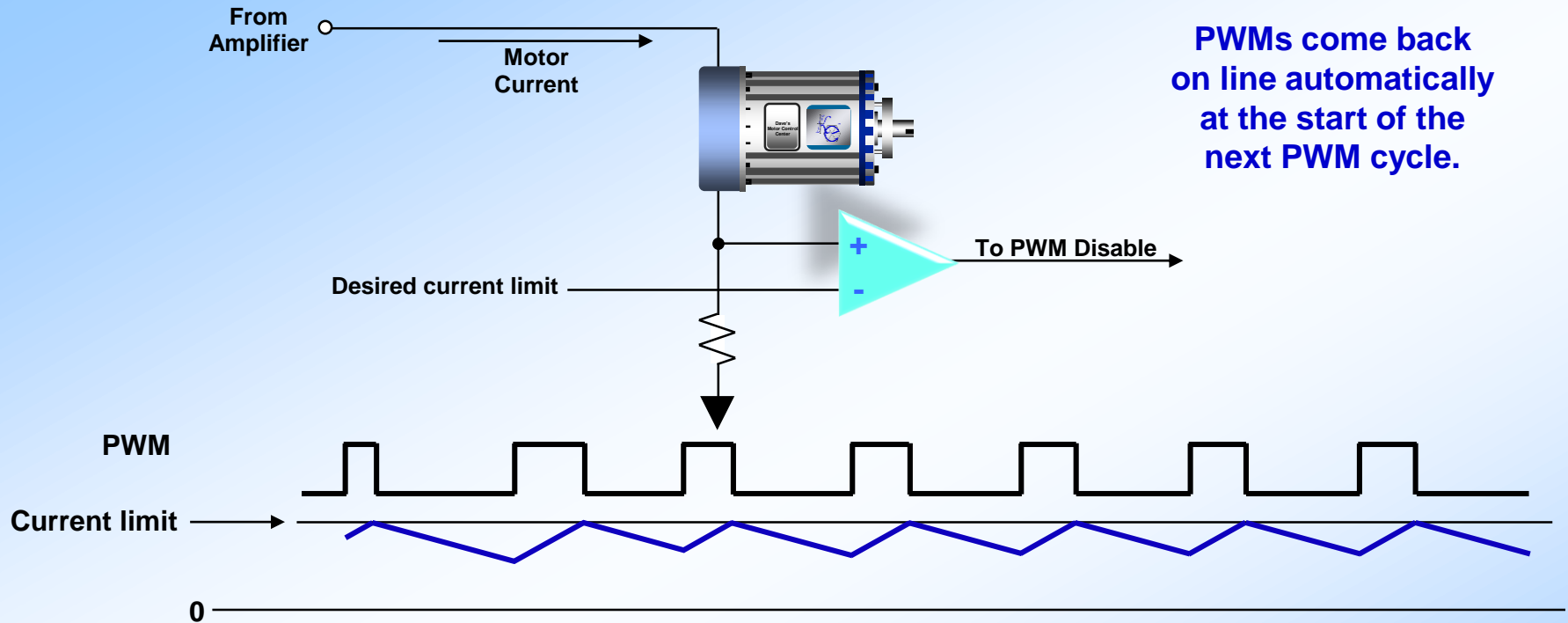


PWMs come back on line automatically at the start of the next PWM cycle.

- Pros:** Great for robust hardware over-current protection.  
Can use on-board hardware comparator and fault inputs on most processors.  
Simple. No software required.  
Cost effective.
- Cons:** Not good for control, since it regulates peak current, not average current.  
Unstable for duty cycles > 50% unless slope-compensation is used.




# In-Line Current Sensing

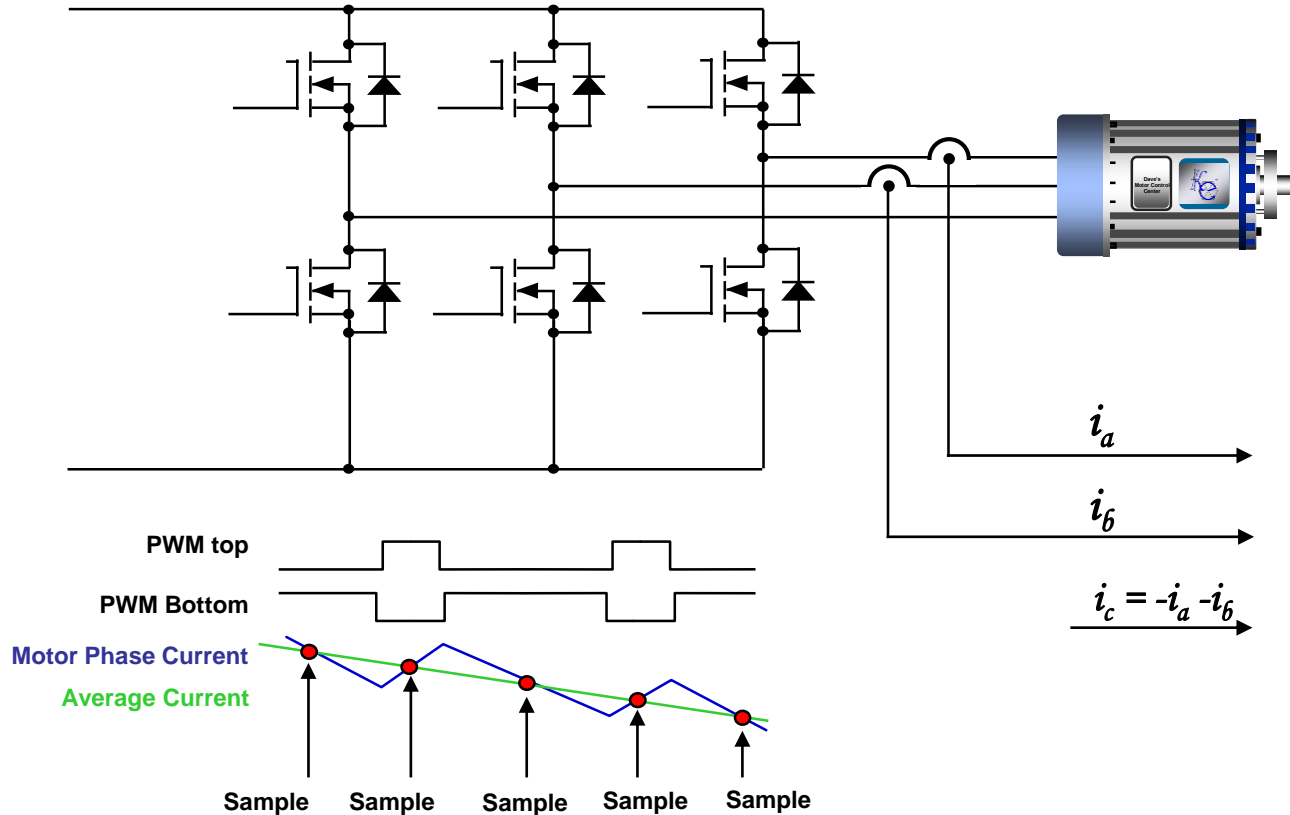

- ✓ Synchronous ADC Sampling helps to filter the measured current – anti-aliasing
- ✓ Noise free ADC sampling when the power transistor is not switching
- ✓ Current signal is ALWAYS visible
- ✓ Current can be sampled at TWICE the PWM frequency (null-vectors V0 AND V7)
- ✓ More expensive!



# LEM Sensors

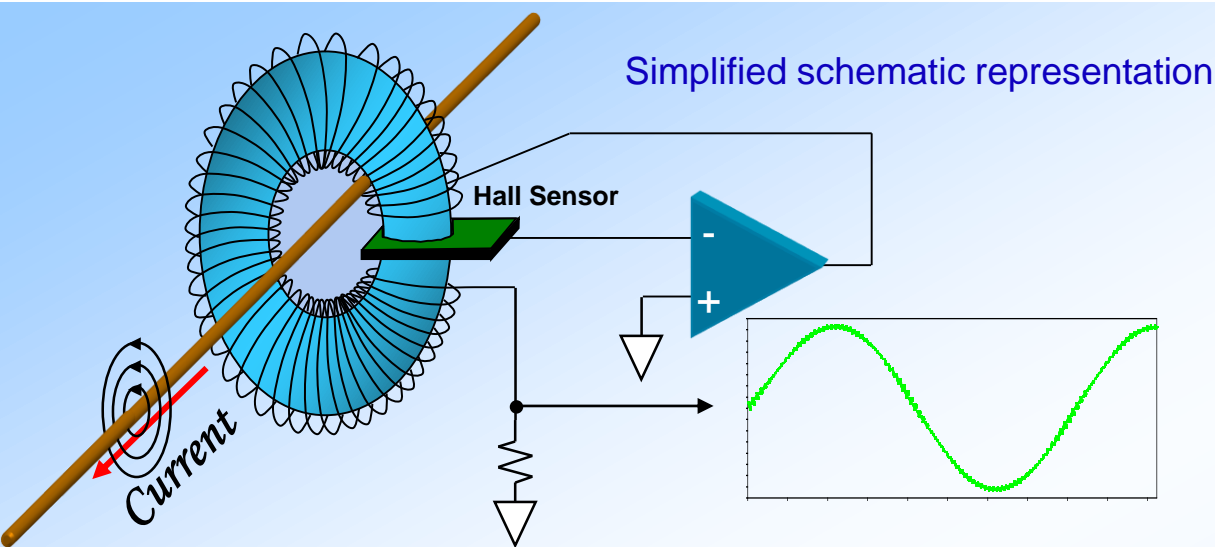

**Most popular in-line current sensing sensor.**

**Excellent linearity (flux is zero, so permeability variations of core material do not affect the linearity of the reading).**


**Frequency response all the way down to DC.**

**Expensive**




# In-Line Current Sampling in Both V0 and V7

Measurements

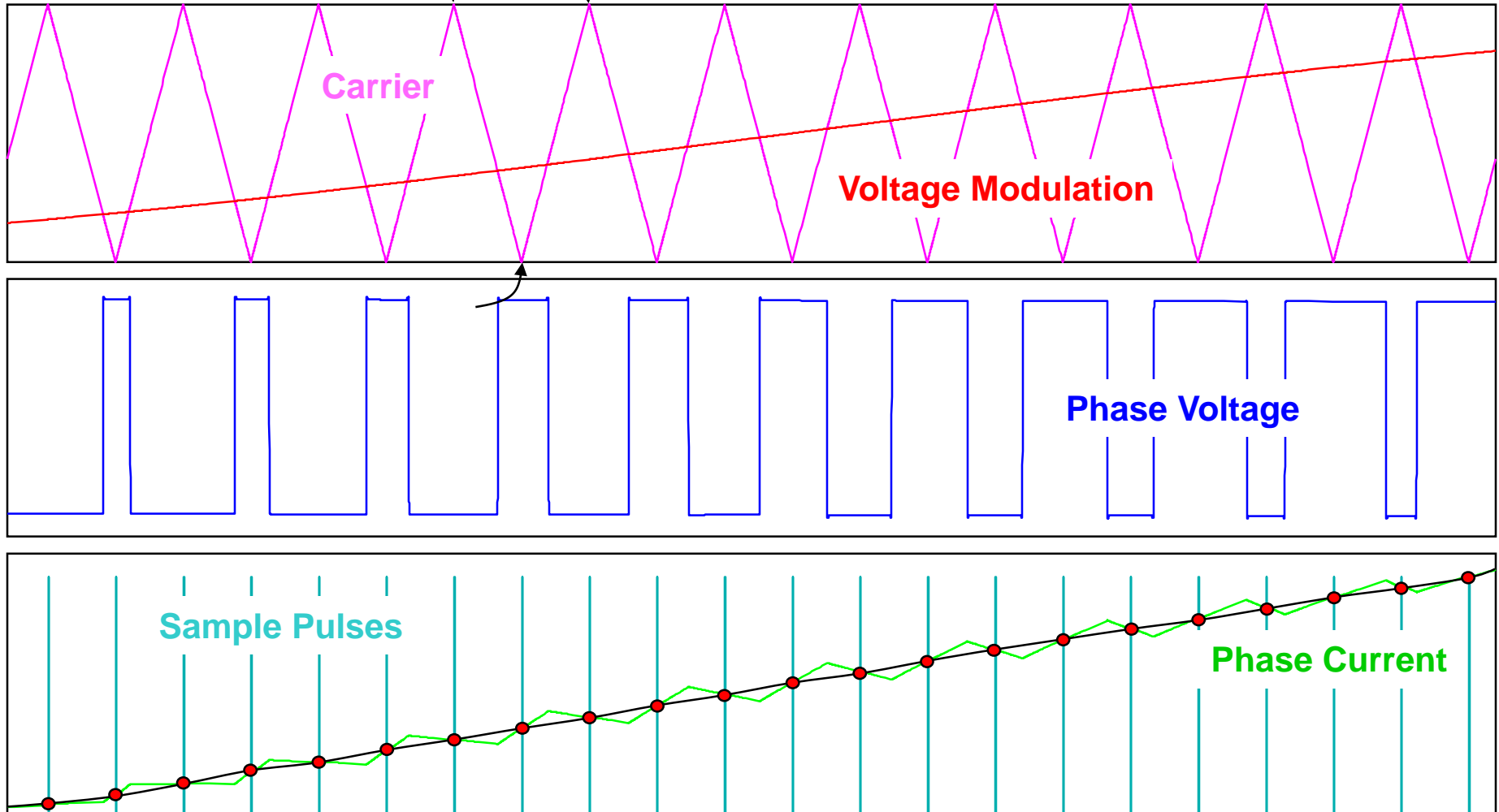

# 2-Shunt Current Sensing

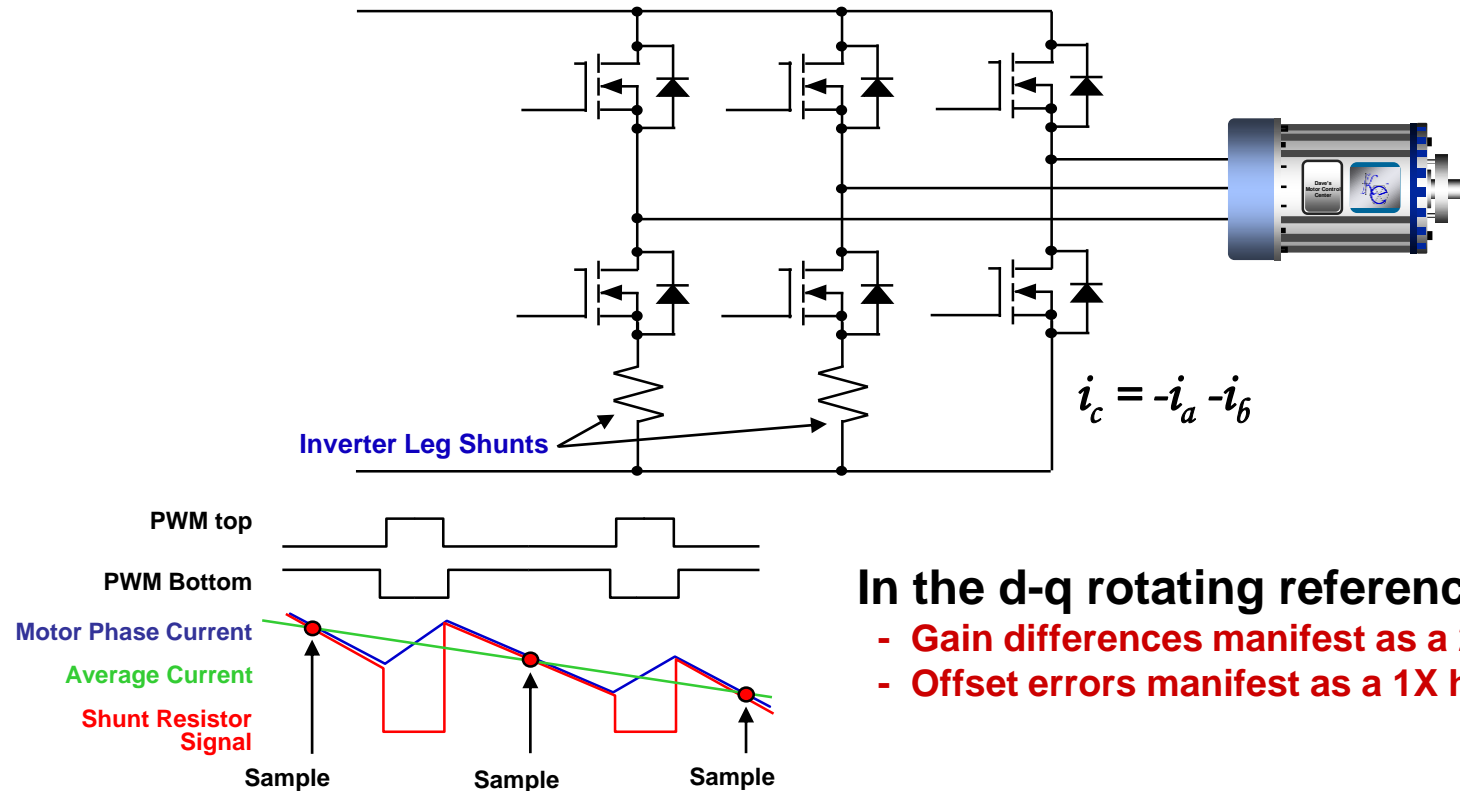


In the d-q rotating reference frame:

- Gain differences manifest as a 2X harmonic distortion
- Offset errors manifest as a 1X harmonic distortion


- ✓ Synchronous ADC Sampling helps to filter the measured current – anti-aliasing
- ✓ Noise free ADC sampling when the power transistor is not switching
- ✓ Current can be sampled at up to the PWM frequency (null-vector V0 only)
- ✓ Current samples are simultaneous.
- ✓ Not suitable for high power motors due to shunt power losses.
- ✓ Reading blackouts occur during high duty-cycle values


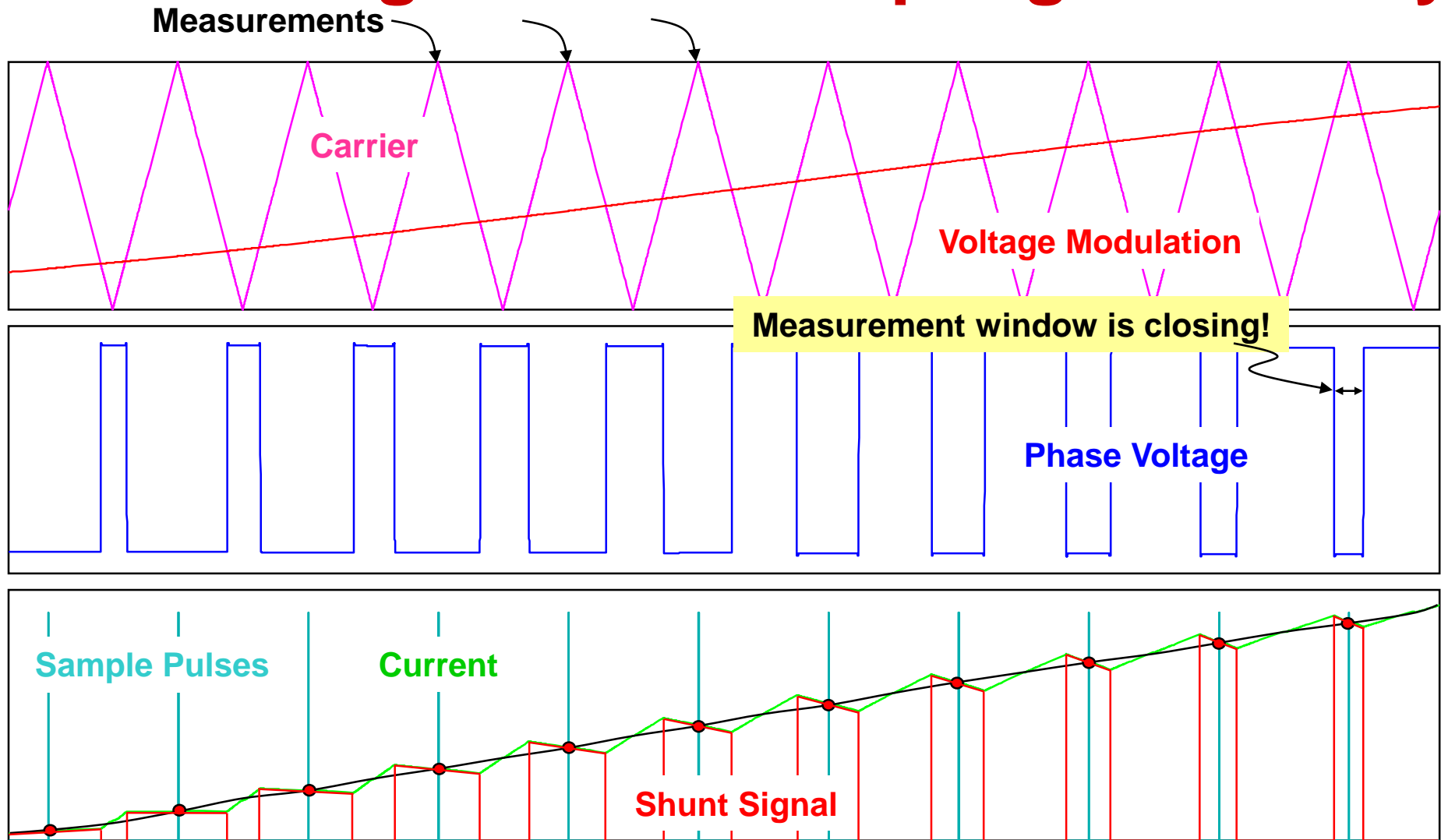
# Inverter Leg Current Sampling in V0 Only



# 3-Shunt Current Sensing

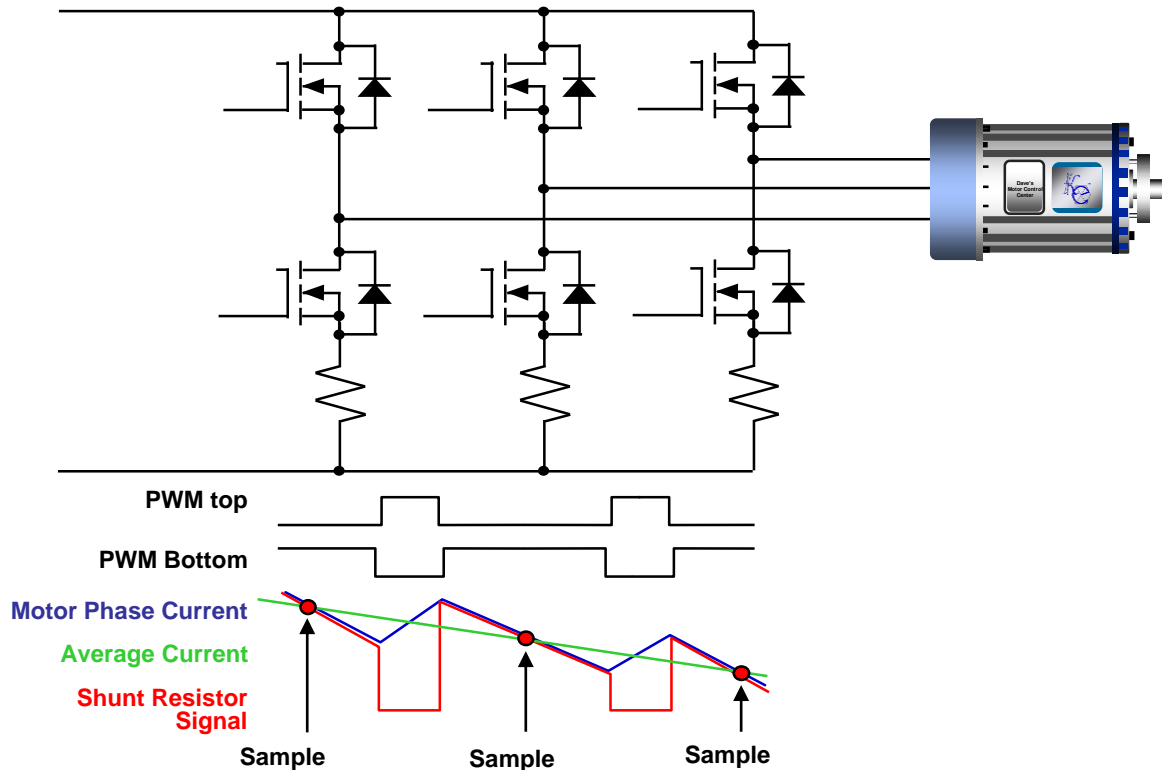


- ✓ Synchronous ADC Sampling helps to filter the measured current – anti-aliasing
- ✓ Noise free ADC sampling when the power transistor is not switching
- ✓ Current can be sampled at up to the PWM frequency (null-vector V0 only)
- ✓ Current samples are simultaneous.
- ✓ 100% Modulation supported by switching between pairs of shunts.
- ✓ Extra shunt results in additional power loss.
- ✓ Channel gain differences can cause waveform discontinuities.





# Selecting Shunt Pairs Based on V-angle

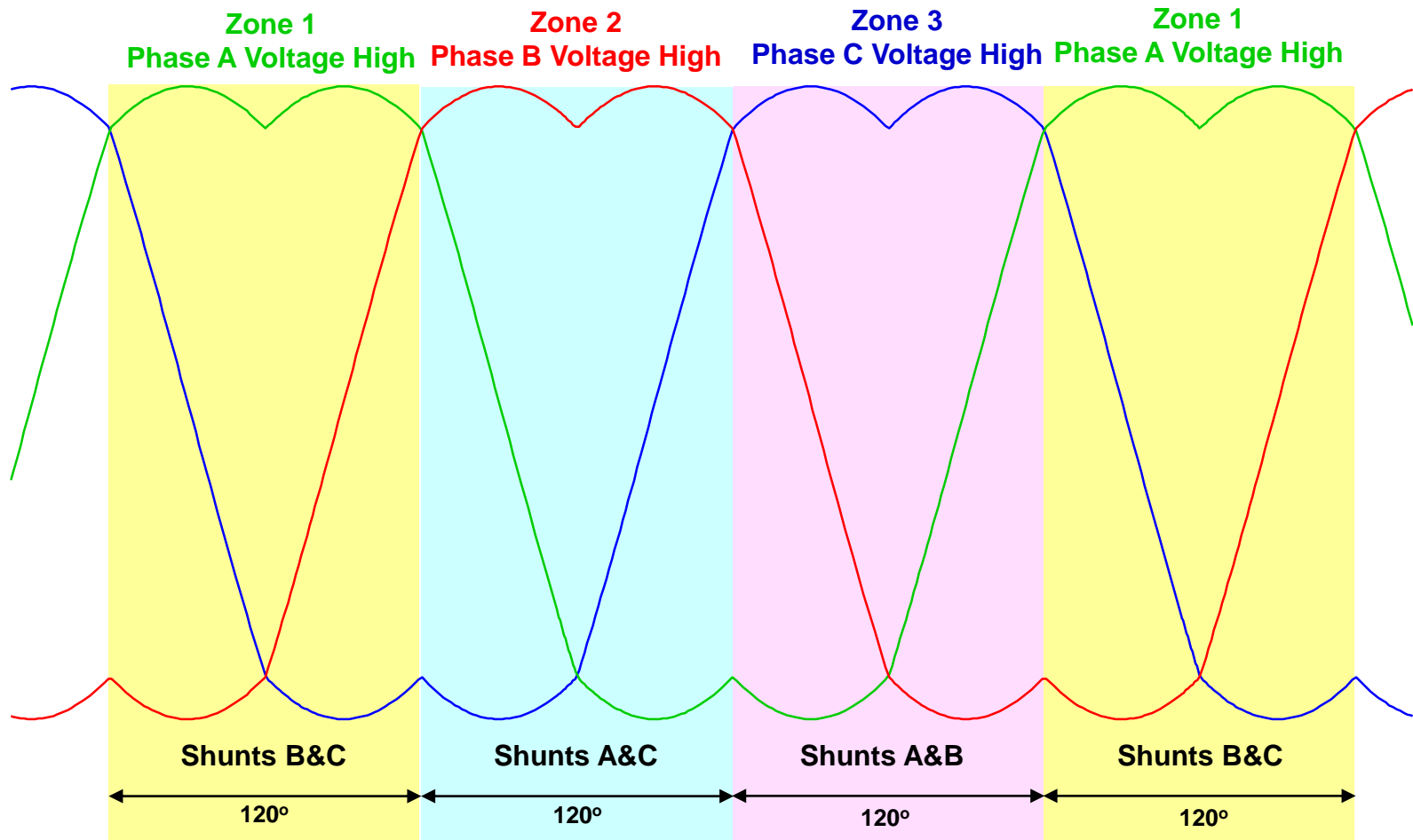


Shunt selections are based on the voltage zones, not the current angles.


Just a one percent gain change from one pair of shunts to the next represents a 41 count discrepancy on a 12-bit converter! Gain calibration may be required.



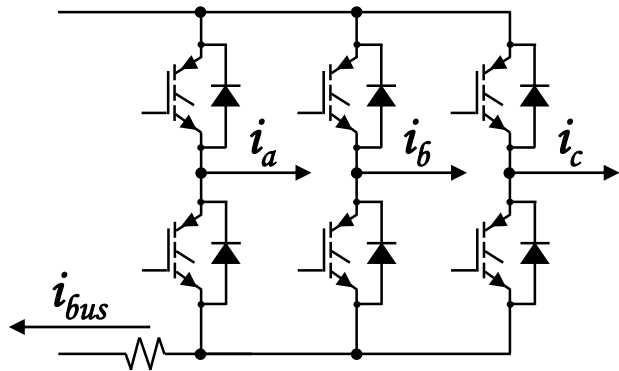
# Phase Current Reconstruction from Single-Shunt Measurement



The inverter can be driven to 8 states.

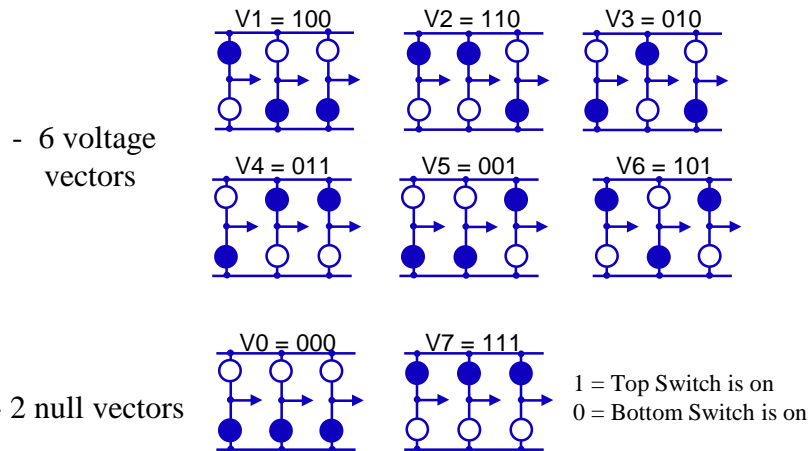


Space Vector	$i_{bus}$ Value
$V1$	$i_a$
$V2$	$-i_c$
$V3$	$i_b$
$V4$	$-i_a$
$V5$	$i_c$
$V6$	$-i_b$

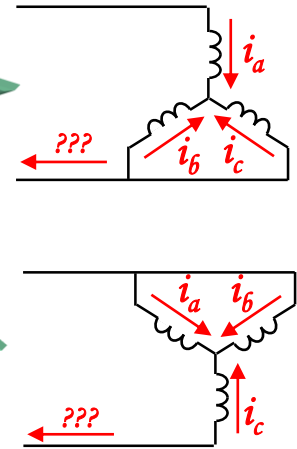

Assumes no ground currents in load

# Single-Shunt Current Sensing

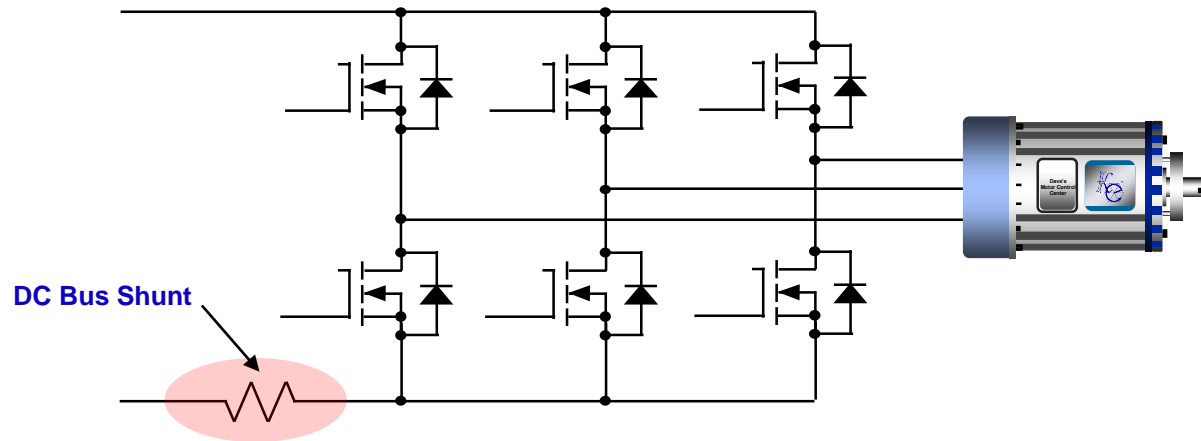

- ✓ Synchronous ADC Sampling helps to filter the measured current – anti-aliasing
- ✓ Noise free ADC sampling when the power transistor is not switching
- ✓ Current can be sampled at SVM periodic rate (TWICE the PWM frequency).
- ✓ Lower power losses due to only one shunt.
- ✓ Only one current amplifier, so no waveform discontinuities due to gain mismatching.
- ✓ Only one shunt and one amplifier represents an economical solution.
- ✓ Op-amp must have much higher slew-rate characteristics.
- ✓ Shunt must be sampled during voltage vectors, NOT null vectors (timers required).
- ✓ ADC triggering is not fixed w.r.t. PWM waveform. (Timer scheduling).
- ✓ Current readings are skewed in time.
- ✓ Reading blackouts occur during similar duty cycles on two or more phases (next slide...)




# Current Sampling Blackout Problem

- **Two current samples cannot be taken when:**


1. voltage vector is crossing Space-vector boundary
  - only one sample can be taken

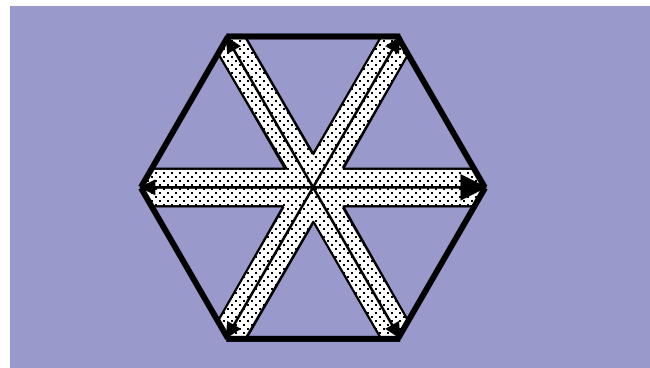1. Areas where voltage vector is crossing SV boundary



2. low modulation indexes
  - sampling intervals are too short
  - none of current samples can be taken

2. **Low Modulation Index**

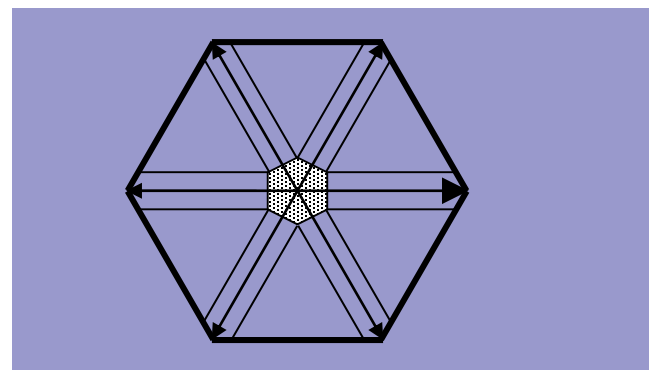


Source: *Freescale Semiconductor*




Keeping your motors **spinning**.

Dave Wilson

# Single-Shunt Waveform

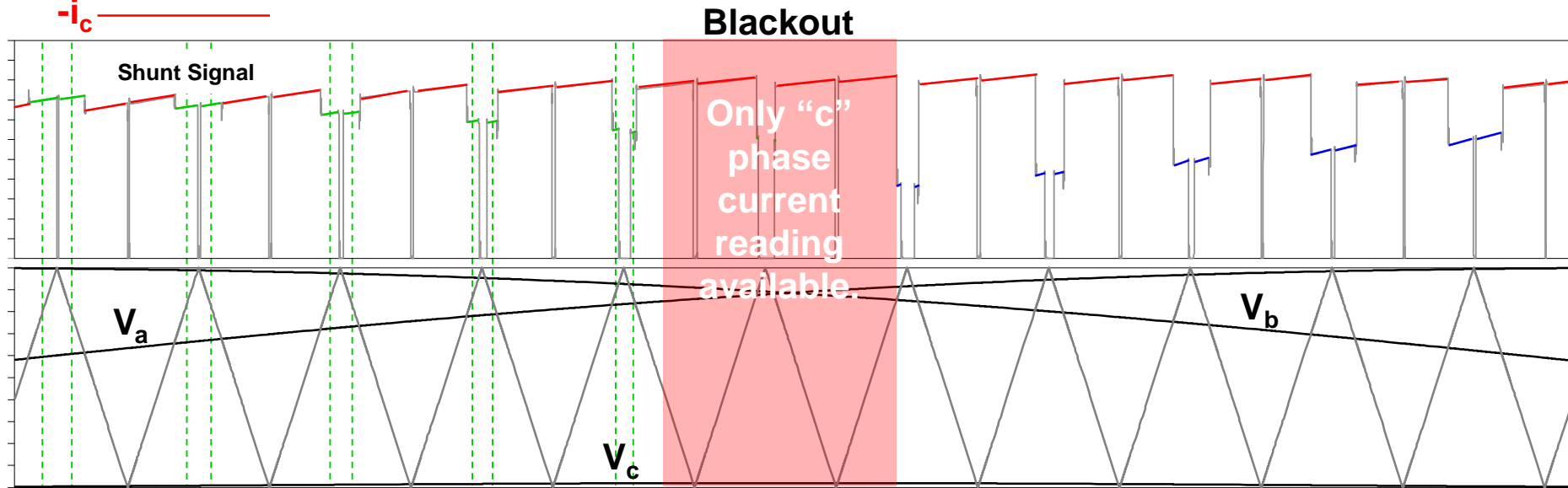

--- Sample interval for "b" current

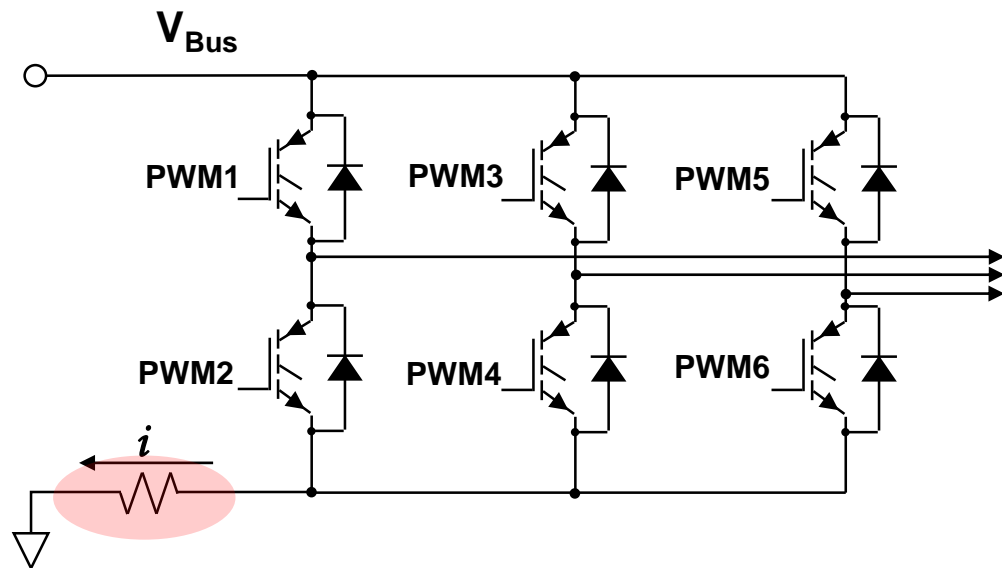


# Single-Shunt Blackout Solutions

## Solution 1:
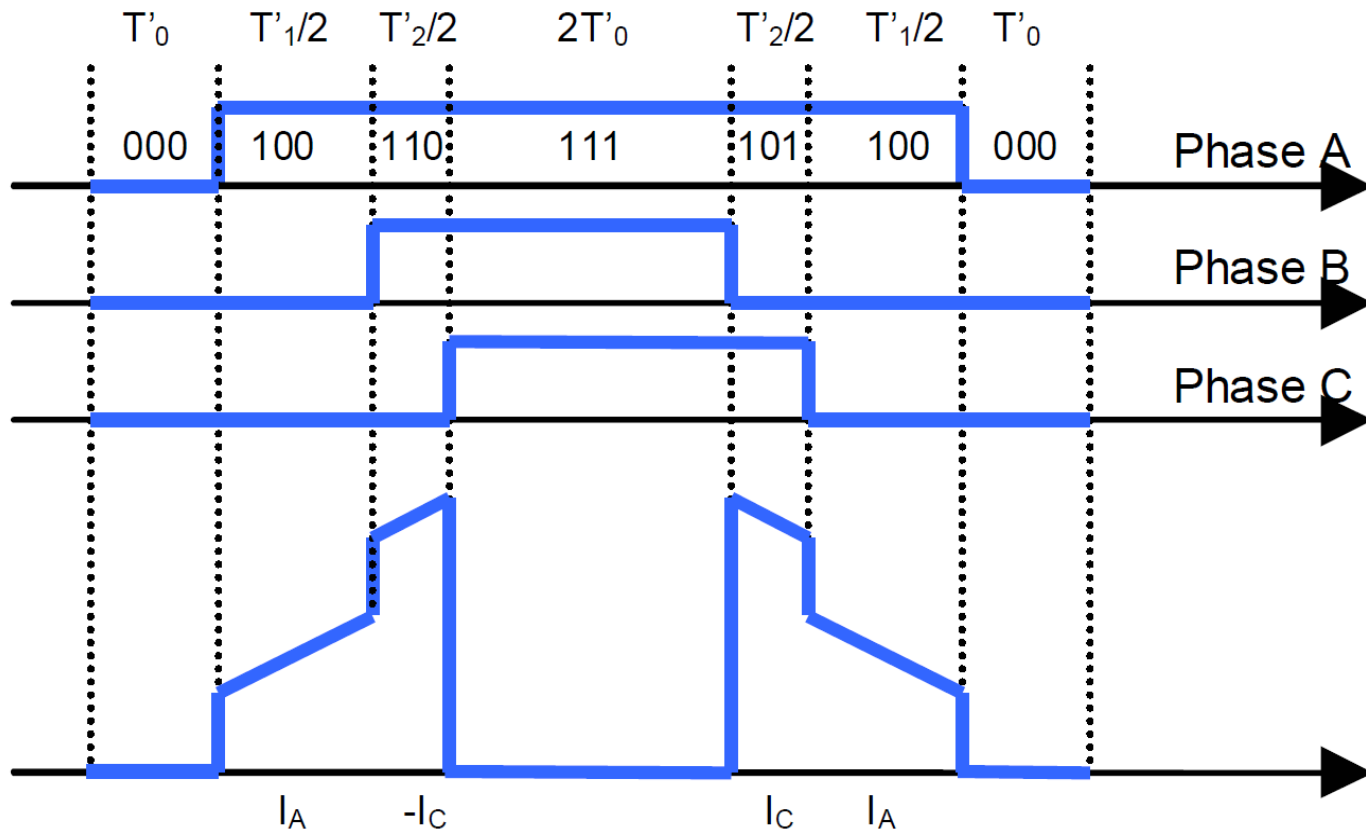
### Asymmetrical PWM

- Modified ON/OFF times
- Duty cycles preserved



Source: STMicroelectronics



Keeping your motors **spinning**.

Dave Wilson


# Single-Shunt Blackout Solutions

## Solution 2:

### Symmetrical PWM – Double Pulse

- Split duty cycle into 2 pulses
- Duty cycles preserved

3-phase visibility!

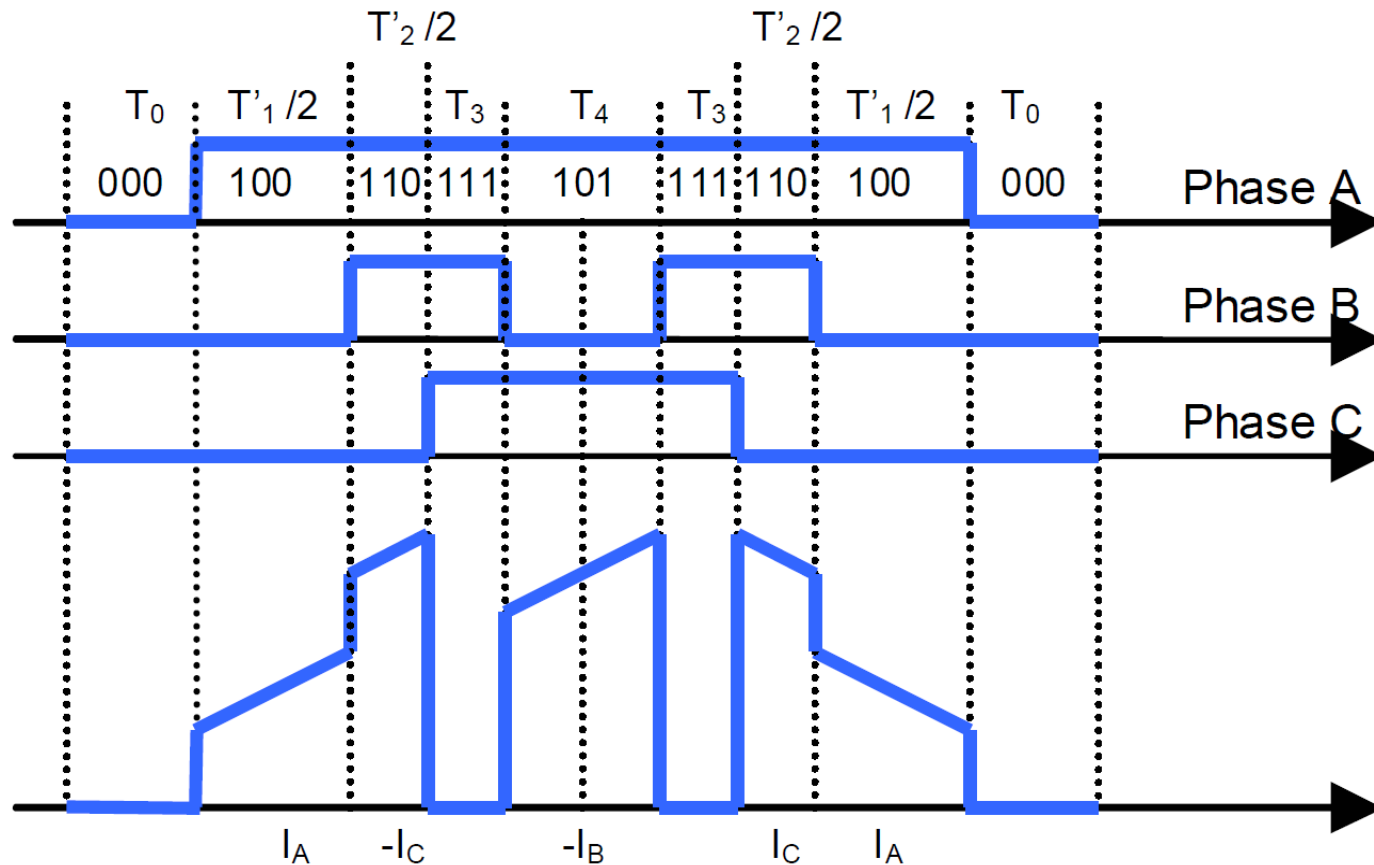


Source: STMicroelectronics



Keeping your motors **spinning**.

Dave Wilson

# Single Supply Bipolar Current Sensing

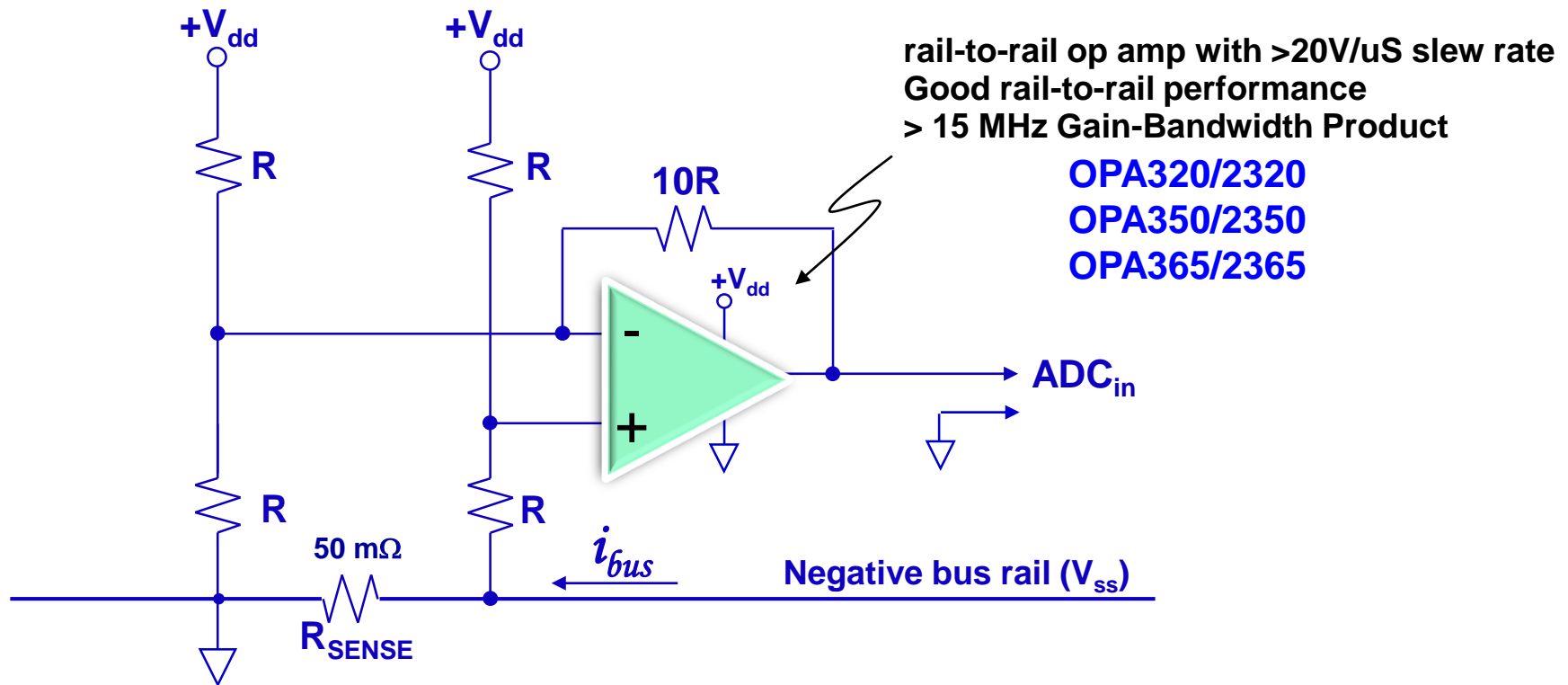

$I_0$  reading is  
taken during  $V_{\text{null}}$  vectors,  
and then stored.

